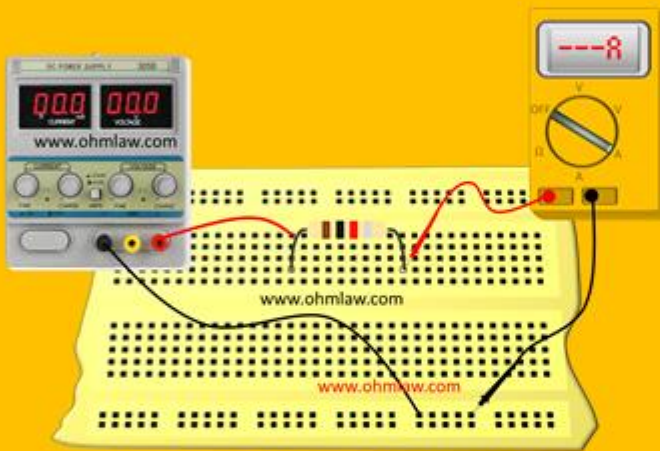


Ohm's law formulas		To Calculate			
		Voltage (V)	Current (I)	Resistance (R)	Power (P)
Given parameters	Current & Resistance	$V = IR$	---	---	$P = I^2R$
	Current & Power	$V = \frac{P}{I}$	---	$R = \frac{P}{I^2}$	---
	Voltage & Current	---	---	$R = \frac{V}{I}$	$P = VI$
	Voltage & Resistance	---	$I = \frac{V}{R}$	---	$P = \frac{V^2}{R}$
	Voltage & Power	---	$I = \frac{P}{V}$	$R = \frac{V^2}{P}$	---
	Power & Resistance	$V = \sqrt{P \cdot R}$	$I = \sqrt{P/R}$	---	---



Digital Library

Electrical and Electronics Engineering

www.electricalandelectronicsengineering.com



Ohm's law

Ohm's law


A fundamental law of Electrical and Electronics Engineering which explains the relationship between current and voltage in circuits

Statement:

For a constant resistance the electrical current flowing through any resistor is directly proportional to voltage applied across it. Mathematically, $V \propto I$

OR

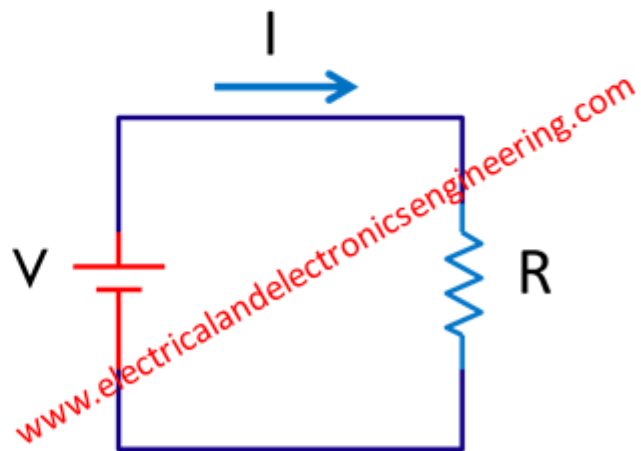The voltage across any resistor equals the current time resistance across it. Mathematically $V = IR$




To learn more about Electrical and Electronics Engineering:

www.electricalandelectronicsengineering.com

An Example

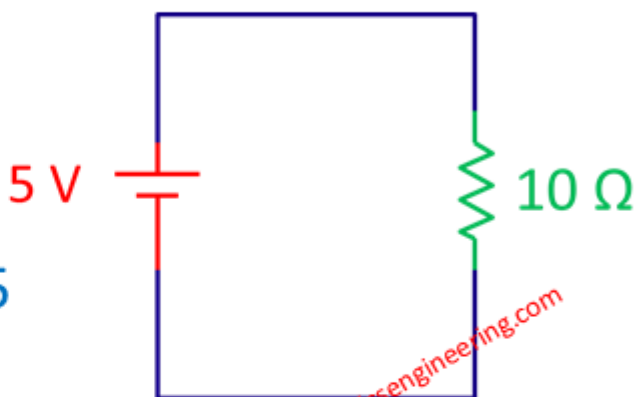Find the current passing through 10 ohms resistor when a voltage source of 5 V connects across it.



$$I = \frac{V}{R} = \frac{5 V}{10 \Omega} = 0.5 A$$



To learn more about Electrical and Electronics Engineering:

www.electricalandelectronicsengineering.com

Other formulas

The electric power flowing through any circuit can be defined as the product of voltage times current passing through it. Mathematically ($P=VI$)

While the above statement is not a statement of Ohm's law, we can utilize it for obtaining some useful equations. Using these we can calculate two of voltage, current, resistance and power from other two known quantities.

Ohm's law formulas		To Calculate			
		Voltage (V)	Current (I)	Resistance (R)	Power (P)
Given parameters	Current & Resistance	$V = IR$	---	---	$P = I^2R$
	Current & Power	$V = \frac{P}{I}$	---	$R = \frac{P}{I^2}$	---
	Voltage & Current	---	---	$R = \frac{V}{I}$	$P = VI$
	Voltage & Resistance	---	$I = \frac{V}{R}$	---	$P = \frac{V^2}{R}$
	Voltage & Power	---	$I = \frac{P}{V}$	$R = \frac{V^2}{P}$	---
	Power & Resistance	$V = \sqrt{P \cdot R}$	$I = \sqrt{P/R}$	---	---




To learn more about Electrical and Electronics Engineering:

www.electricalandelectronicsengineering.com


Ohm's law Experiment

Ohm's law can be easily verified using the experiment:

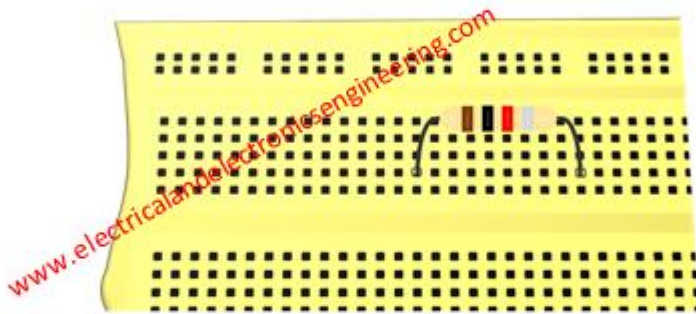Step 1: Connect a resistor of 1kohm on breadboard



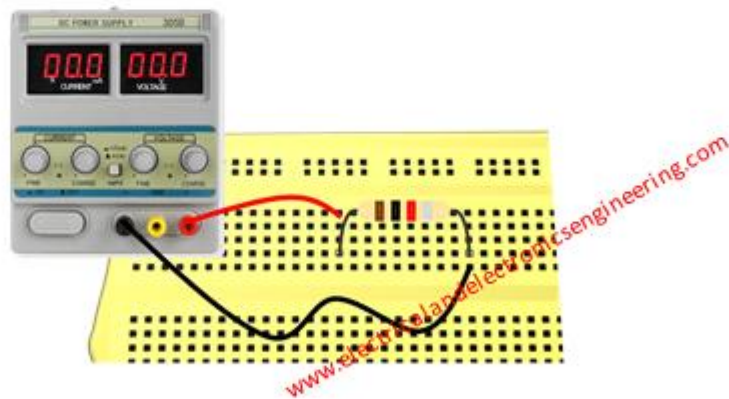Step 2: Connect a variable DC Power supply across it




To learn more about Electrical and Electronics Engineering:


www.electricalandelectronicsengineering.com

Ohm's law Experiment

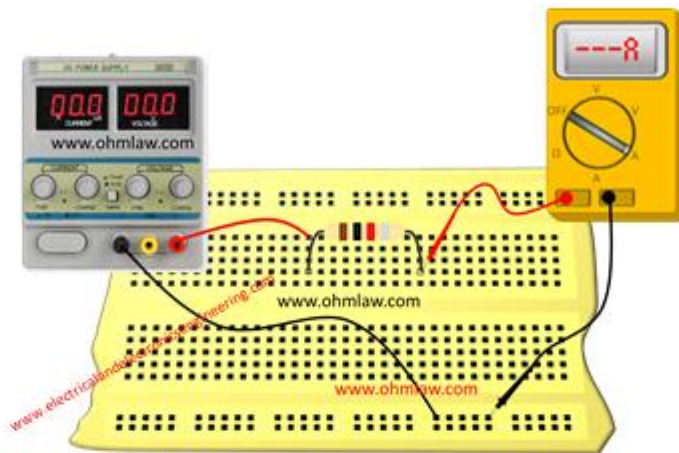Step 3: Connect ammeter in series of circuit



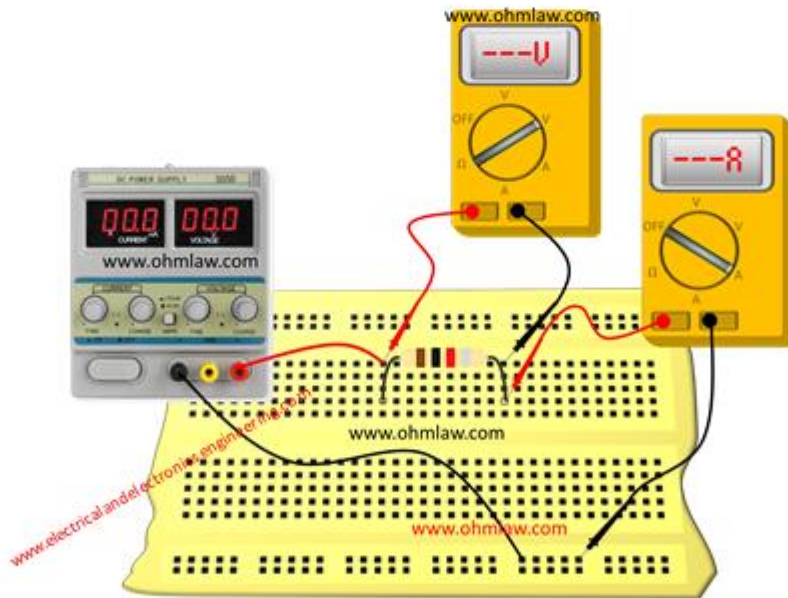Step 4: Connect voltmeter in parallel to the resistor



To learn more about Electrical and Electronics Engineering:

www.electricalandelectronicsengineering.com

Ohm's law Experiment

Step 5: Apply 1 volt to resistor and take reading from ammeter

Step 6: Increase the voltage by 1 V and measure current

Step 7: Repeat the same steps from 1 V to 10 V and measure the current

Note the observations, finally you'll obtain a table like this:

Voltage	Current
1 V	1 mA
2 V	2 mA
3 V	3 mA
4 V	4 mA
5 V	5 mA
6 V	6 mA
7 V	7 mA
8 V	8 mA
9 V	9 mA
10 V	10 mA




To learn more about Electrical and Electronics Engineering:

www.electricalandelectronicsengineering.com

Ohm's law Experiment

Let's sketch a graph for the readings:

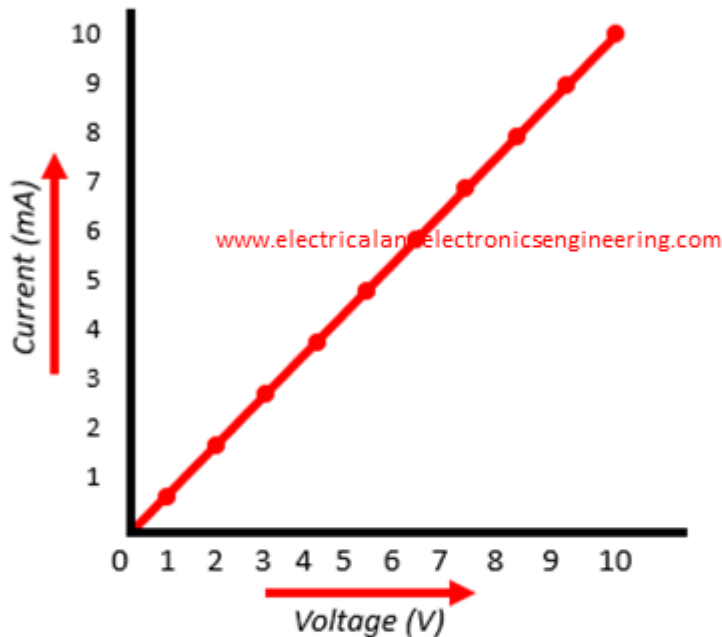

As you can see the graph for Ohm's law is a linear straight line. This proves the direct relationship between voltage and current for a constant resistor



To learn more about *Electrical and Electronics Engineering*:

www.electricalandelectronicsengineering.com

Surf hundreds of Books in our Digital Library



Digital Library

Electrical and Electronics Engineering
www.electricalandelectronicsengineering.com

EEE Ohm's law



Digital Library

Electrical and Electronics Engineering
www.electricalandelectronicsengineering.com

EEE Components of Transmission Lines



Digital Library

Electrical and Electronics Engineering
www.electricalandelectronicsengineering.com

EEE Switchgear



Digital Library

Electrical and Electronics Engineering
www.electricalandelectronicsengineering.com

EEE Transformer Types



Digital Library

Electrical and Electronics Engineering
www.electricalandelectronicsengineering.com

EEE Basic Electrical Formulas



Digital Library

Electrical and Electronics Engineering
www.electricalandelectronicsengineering.com

EEE Current transformer



Digital Library

Electrical and Electronics Engineering
www.electricalandelectronicsengineering.com

EEE Potential transformer



Digital Library

Electrical and Electronics Engineering
www.electricalandelectronicsengineering.com

EEE Induction Motor MCQs



Digital Library

Electrical and Electronics Engineering
www.electricalandelectronicsengineering.com

EEE Insulation Resistance & IR Testing of cables



Electrical and Electronics Engineering

E

No part of this book can be reproduced, stored, transmitted, in any form or in any means without prior written permission.

Where not mentioned the Photos/Images and any other diagrams in this E-book are from CC0 sources.

E

The data provided in Electrical and Electronics Engineering E-book comes without any guarantee/warranty. We don't intent to provide practical DIY tutorials.

We provide information so that you can better understand and develop basic concepts on various EEE topics.

E

Books in our Digital Library are produced by Electrical and Electronics Engineers, DIY Electrical Learners, Hobbyists, and our fans.

For any errors/typo or mistakes please report us.